

98 Number Page 6 Figure 6: Address Map

Page 100

A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀		RAM CHIPS
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1 st	RAM CHIP 0
0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	Last	
0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1 st	RAM CHIP 1
0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	Last...	
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1 st	RAM CHIP 2
0	0	0	0	1	0	1	1	1	1	1	1	1	1	1	1	Last	
0	0	0	0	1	1	0	0	0	0	0	0	0	0	0	0	1 st	RAM CHIP 3
0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	Last	

Draw the diagram of 8-bit microprocessor with 16 bit address bus interfaced with 7KB RAM **using the full decoding technique**. Each RAM chip has 10 bit address bus and 8 bit data bus. Also provide the corresponding address map for each RAM chip.

Ans:

Page 7/101

Given,
RAM Chip

Address Bus = 10 bit

Data Bus = 8 bit

$$\begin{aligned}\text{Memory size of a single RAM chip} &= 2^{10} \times 8 \\ &= 8192 \text{ bits} \\ &= \frac{8192}{8} \text{ bytes} \\ &= 1024 \text{ bytes} \\ &= \frac{1024}{1024} \text{ KB} \\ &= 1 \text{ KB}\end{aligned}$$

$$\text{Target} = 8 \times 1 \text{ KB}$$

Which mean we will need 8 RAM chips.

$$\begin{aligned}\text{Memory size / Capacity of the Processor} &= 2^{16} \times 8 \text{ bits} \\ &= 524288 \text{ bits} \\ &= \frac{524288}{8} \text{ bytes} \\ &= 65536 \text{ bytes} \\ &= \frac{65536}{1024} \text{ KB} \\ &= 64 \text{ KB.}\end{aligned}$$

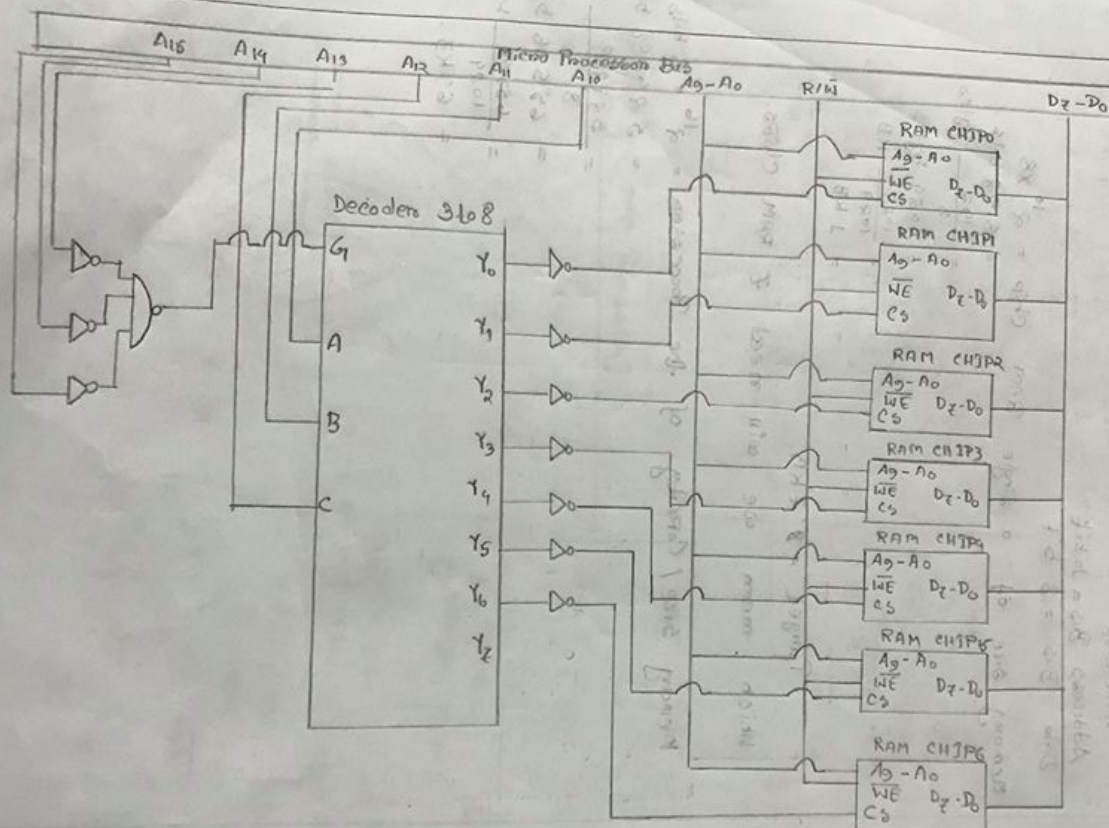


Fig: Micro Processor Interfaced with 8K RAM

* DeCode নাগানোর ক্ষেত্রে কিছুক্ষণ বাকি থাকে যেখানে ০
বাকি রাখা হয়, এ চিপস দ্বারা Active করে ফেলে
Microprocessor hang করে,

Slide → 8255 PPI

Q Draw 8255 NP diagram.
Ans

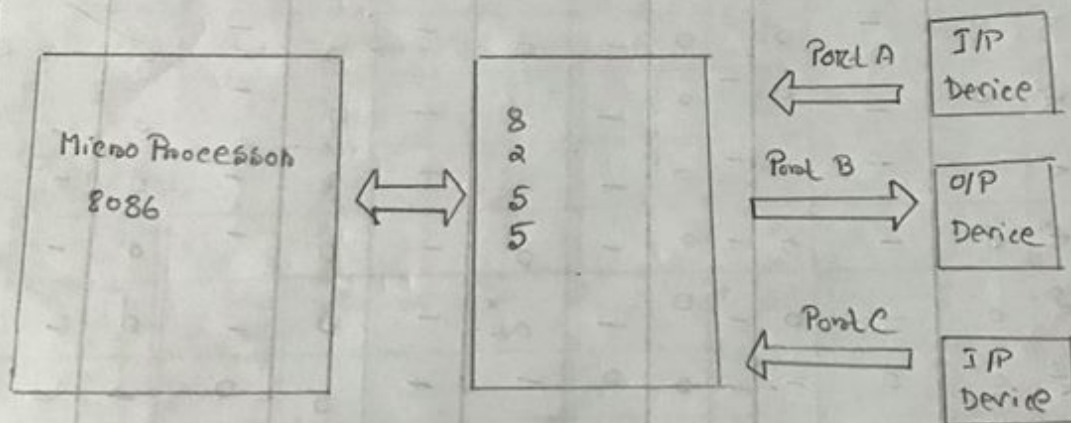


Fig 8086 NP diagram

* PPI তে ২৭ টা I/O Pins আছে, যেখানে ১২টা
programmable group Pin.
* PPI ৩ টা different mode ত কাজ করে,

Mode 0	Basic I/O
Mode 1	Strobe I/O
Mode 2	Bi-directional bus

Mode 0:

Port A, B & C can work either as input function or as output function.

Mode 1:

In this either Port A or B can work & Port C bits are used to provide handshaking.

Mode 2:


In this mode only Port A will work, Port B can either be in Mode 0 or 1 & Port C bits are used as handshake signal.

Device Mode to operate are:

1. Peripheral Device I/O \Rightarrow MODE 0
2. 7 Segment Display \Rightarrow MODE 0
3. Single Push button \Rightarrow MODE 0
4. Matrix keyboard \Rightarrow MODE 0
5. PC keyboard \Rightarrow [ASCII]
6. Printer \Rightarrow [ASCII]
7. Embedded System LCD Display \Rightarrow MODE 0
8. PC LCD \Rightarrow MODE 1.

- * PC keyboard \Rightarrow ASCII key Value send করে,
- * Single Push button \Rightarrow High/Low Voltage send করে,
- * MODE 1 \Rightarrow Acknowledgement এর সুবিধা আছে,
Hand shaking এর মাধ্যমে কাজ করা,

82C55 Pin Layout

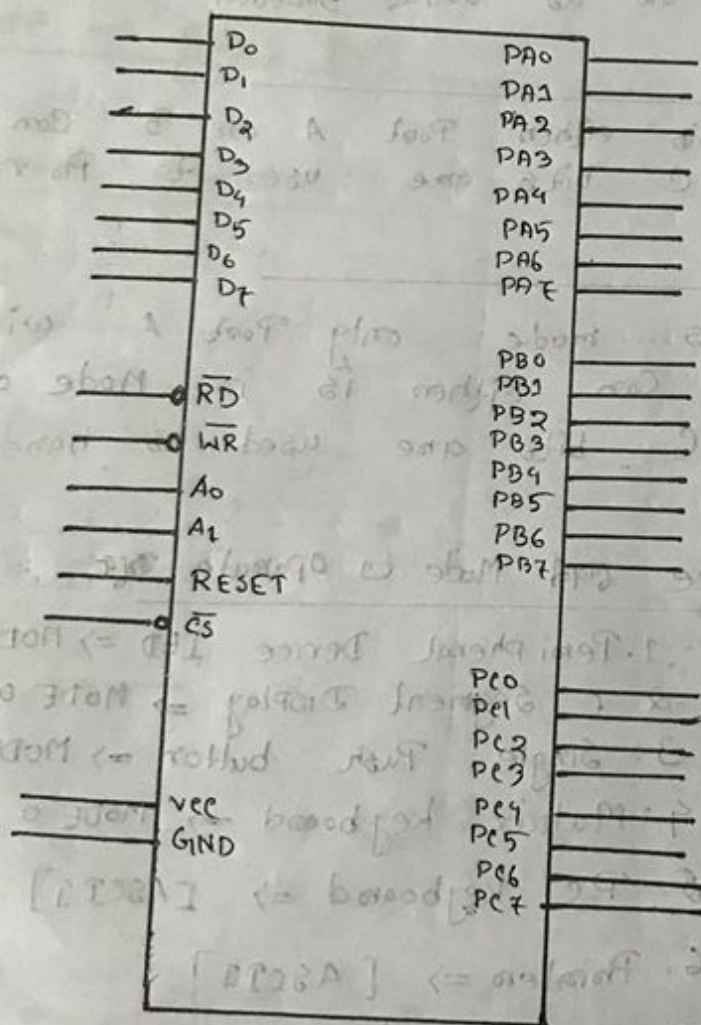

GROUP A $\Rightarrow (PA_7 - PA_0) \text{ \& } (PC_7 - PC_4)$
 GROUP B $\Rightarrow (PB_7 - PB_0) \text{ \& } (PC_3 - PC_0)$


* A_0 & A_1 Pin द्वारा कोई Port Active और Select

A_1	A_0	Function
0	0	Port A
0	1	Port B
1	0	Port C
1	1	Command Register


* Command Byte MODE 1 \Rightarrow MODE 0 to 1011

Programming 82C55

Command Byte A (Program Ports A, B, C)

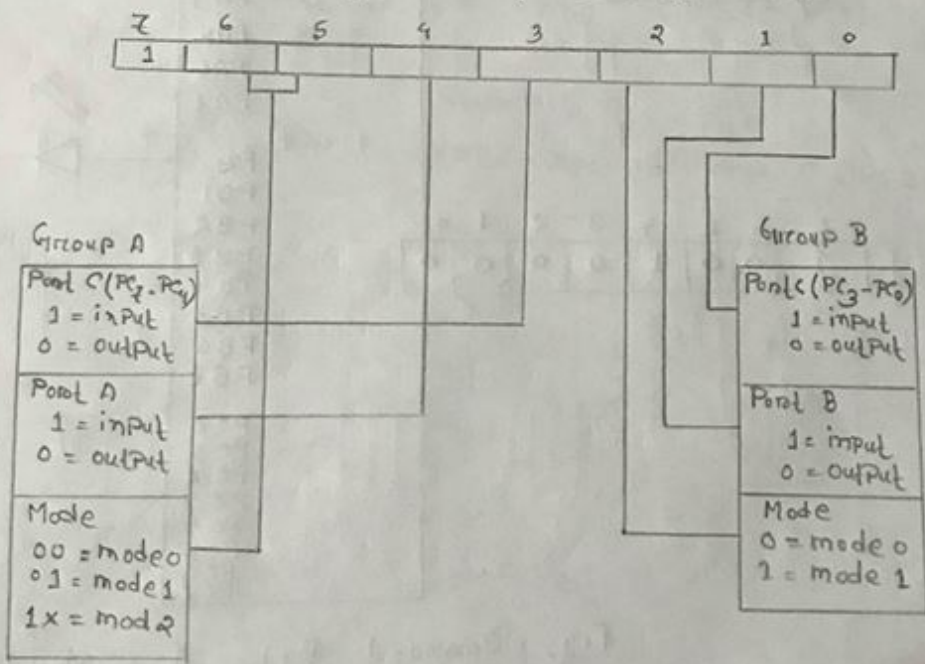

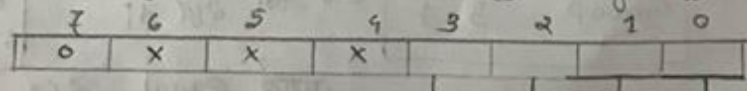Command Byte B (Sets or Resets any bits in Port C)



Bit Set/Reset
1 = Set
0 = Reset

Suppose you want to interface push button with Peripheral interface 8255 Port A & LED with Peripheral interface 8255 Port B. Write down the appropriate Command byte for A for 8255 Command Register.

Ans.

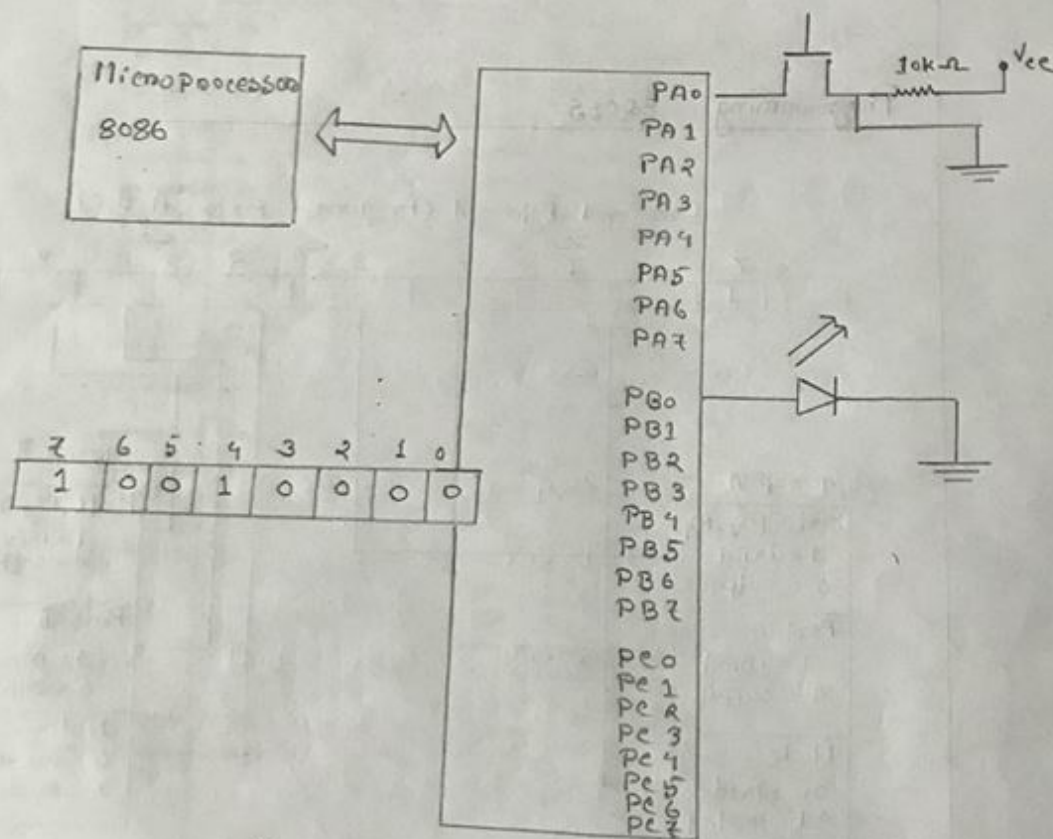


Fig: Command Byte A = 0b 100 10000

Group A = 0
Group B = 1

→ Input device




अथवा equal device

Group A = 1
Group B = 0

→ Output device

Input → Read करवा
Output → Send करवा high/low voltage.


Basic Mode Definitions & Bus Interface

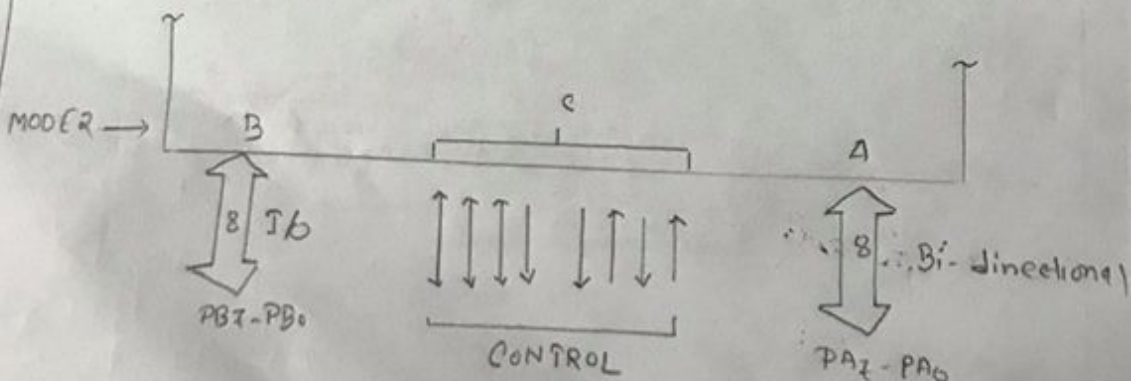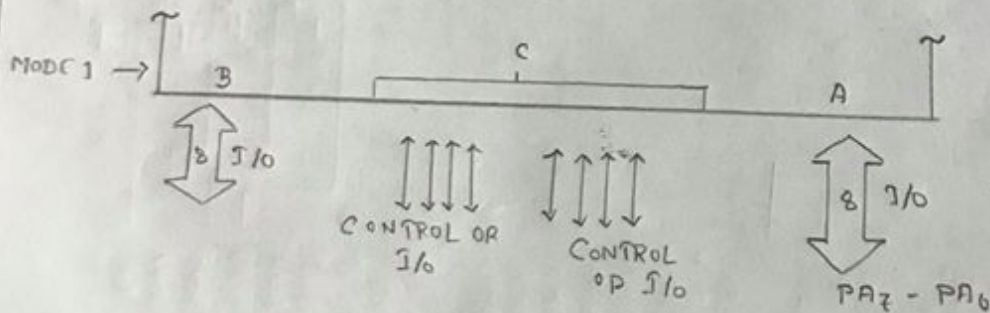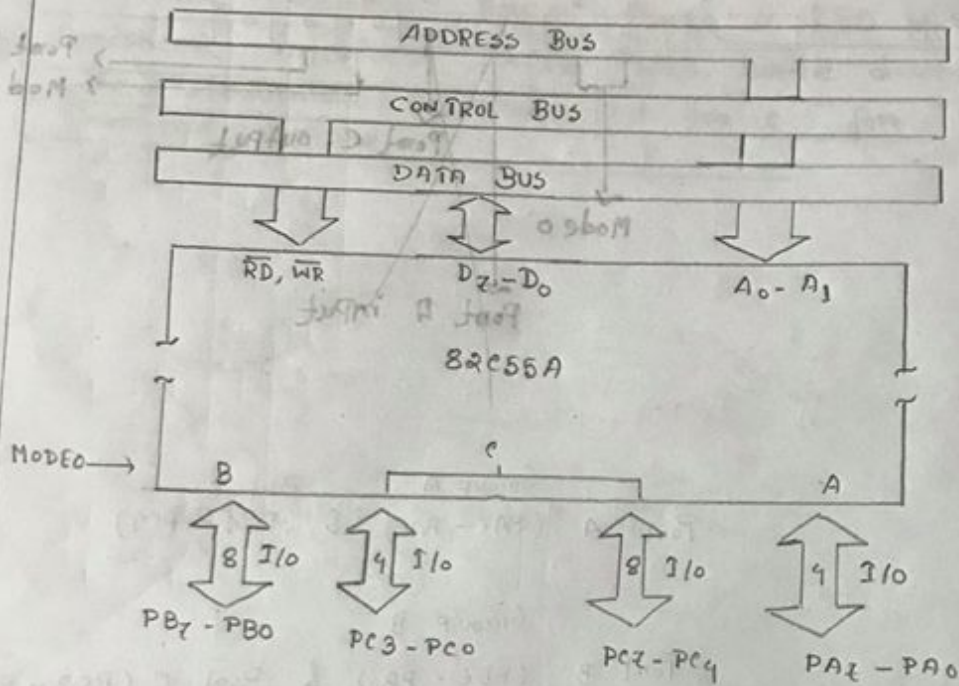

Q Write notes on Basic Input/Output [Mode 0]

Ans:

- This functional Configuration Provides simple input & output operations for each of the three Ports.
- No handshaking is required, data is simply written to or read from a specified Port.

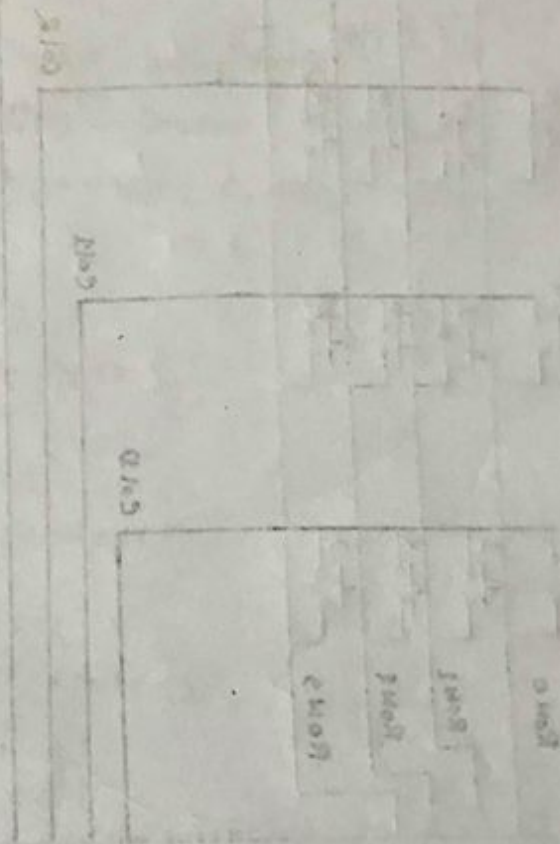

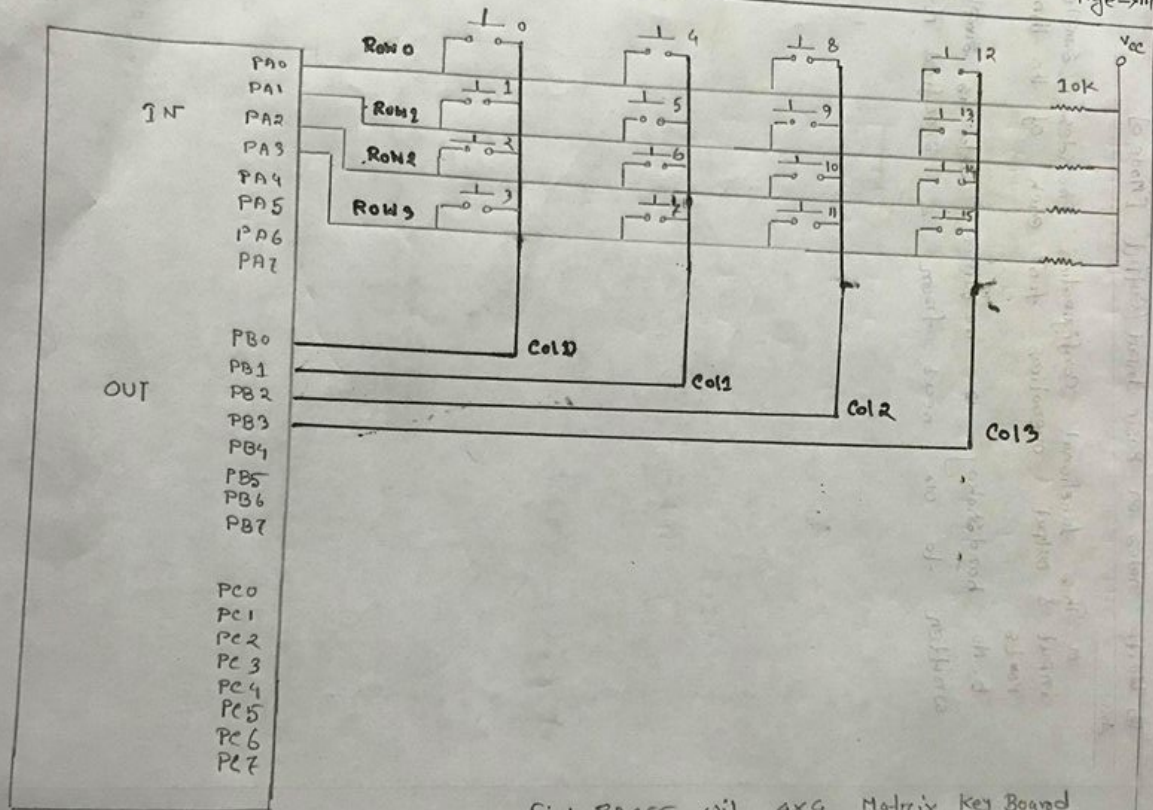


Fig: 82C55 with 4x4 Matrix Key Board

16 switch বিলিফ (1x4) matrix keyboard 8255 এর
Port A এর Port B এর সাথে interface করা করছে।

* প্রতিটা row 0.5V এর Vcc এর সাথে Connected.
এই Connection এর মাধ্যমে রয়েছে 10K-এ Pull up
resistor. Resistor লাগানো হয়, যেন row যখন
Pull high নাহলে,

* Port B এর 0 Volt.

* Button Press করলে Low Voltage.

* 8255 Column স্বীকৃতি Inread এ প্রতিক্রিয়া দেয়।

* Voltage যখন high হলে Current flow করে না

Looping

```

if (PA0 == 0) {
    execute();
}
if (PA1 == 0) {
    execute();
}
if (PA2 == 0) {
    execute();
}
if (PA3 == 0) {
    execute();
}

```



```
if (PB1 == LOW && PA0 == LOW) {  
    Print "Button 4";  
}
```

```
if (PB1 == LOW && PA1 == LOW) {  
    Print "Button 5";  
}
```

```
if (PB1 == LOW && PA2 == LOW) {  
    Print "Button 6";  
}
```

```
if (PB1 == LOW && PA3 == LOW) {  
    Print "Button 7";  
}
```

Write algorithm (flowchart for 4x4 Matrix keyboard)

Ans

